

**Model Question Paper**  
**Semiconductor devices and their applications - Part IV**

12th Standard

**Physics**

Reg.No. : 

--	--	--	--	--	--

I. Answer all questions.

II. Use blue pen only.

Time : 01:00:00 Hrs

Total Marks : 75

5 x 1 = 5

**Part-A**

- 1) The Boolean equation of EXOR gate is  $Y = A \oplus B =$   
(a)  $AB + \bar{B}\bar{A}$  (b)  $AB + \bar{A}\bar{B}$  (c)  $\bar{A}\bar{B} + AB$  (d)  $\bar{A}\bar{B} + \bar{A}B$
- 2) The voltage gain if the non-inverting amplifier is  
(a)  $A_V = \frac{-R_f}{R_{in}}$  (b)  $A_V = 1 + \frac{R_f}{R_{in}}$  (c)  $A_V = 1 - \frac{R_{in}}{R_f}$  (d)  $A_V = \frac{R_f}{R_{in}} - 1$
- 3) In a non-inverting amplifier  $R_{in} = 10 \text{ k}\Omega$  and  $R_{in} = 490 \text{ k}\Omega$  then its voltage gain is  
(a) 49 (b) 50 (c) 4900 (d) 500
- 4) The gain of the amplifier is 100. If 9% of the output voltage is fed back into the input through a negative feedback network. Find out the voltage gain after feedback.  
(a) 10 (b) 16.66 (c) 11.11 (d) 1000
- 5) Simple form of Boolean expression  $A \cdot \bar{B} + AB + BC + CA$  is  
(a)  $(A+B)C$  (b)  $(AB+C)$  (c)  $A+(BC)$  (d)  $ABC$

**Part-B**

3 x 3 = 9

- 6) In a common base transistor circuit  $I_C = 0.97 \text{ mA}$  and  $I_B = 30 \mu\text{A}$ . Calculate the value of  $(\alpha)$  current gain.
- 7) The voltage gain of an amplifier without feedback is 100. If negative feedback is applied with a feedback fraction  $\beta = 0.1$ . Calculate the voltage gain after feedback.
- 8) When there is no feedback, the gain of the amplifier is 100. If 5% of the output voltage is fed back into the input through a negative feedback network, find out the voltage gain after feedback.

**Part-C**

3 x 5 = 15

- 9) Define current amplification factors  $\alpha$  and  $\beta$  and obtain the relation between them.
- 10) With the circuit diagram, explain voltage divider biasing of a transistor.
- 11) Describe the construction of Zener diode.

**Part-D**

5 x 10 = 50

- 12) Give the function of 'OR' and 'NAND' gates.
- 13) Describe an operational amplifier. Explain its action as (i) inverting amplifier and (ii) non-inverting amplifier.
- 14) Explain with neat circuit diagram, the working of single stage CE amplifier. Draw the frequency response curve and discuss the results.
- 15) a) Describe the working of a single stage CE amplifier

**(OR)**

- b) What is meant by feedback? Derive an expression for voltage gain of an amplifier with negative feedback.

\*\*\*\*\*