

Model Question Paper
Semiconductor devices and their applications - Part II

12th Standard

Physics

Reg.No. :

--	--	--	--	--	--

I. Answer all questions.

II. Use blue pen only.

Time : 01:00:00 Hrs


Total Marks : 100

3 x 1 = 3

Section-A

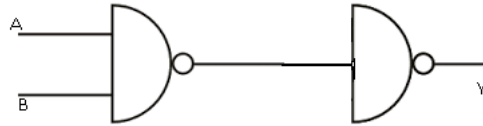1)


The following arrangement performs the logic function of _____ gate



- (a) AND (b) OR (c) NAND (d) EXOR

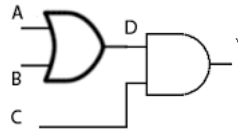2)

If the output (Y) of the following circuit is 1, the inputs A B C must be



- (a) 0 1 0 (b) 1 0 0 (c) 1 0 1 (d) 1 1 0

3) The Boolean expression \overline{ABC} can be simplified as

- (a) $AB + \overline{C}$ (b) $\overline{A} \cdot \overline{B} \cdot \overline{C}$ (c) $AB + BC + CA$ (d) $\overline{A} + \overline{B} + \overline{C}$


Section-B

4) Give the important parameters of an operational amplifier.

2 x 3 = 6

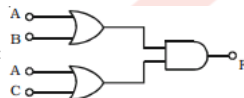5)

Find the output F of the logic circuit given below:




Section-C

3 x 3 = 9

6) The base current of the transistor is $50 \mu A$ and collector current is 25 mA. Determine the values of β and α .

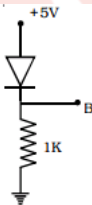7)

Find the voltage at the point B in the figure (Silicon diode is used).




8) The gain of an amplifier, without feedback is 100. If 5% of the output voltage is feed back into the input through a negative feed back network. Find out the voltage gain after feed back.

Section-D

2 x 5 = 10

9) Determine the frequency of oscillations in a Colpitt's oscillator if $C_1 = 0.01 \mu F$, $C_2 = 0.03 \mu F$ and $L = 100 \text{ mH}$.

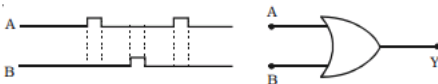10) If the two waveforms shown in the figure are applied to the OR gate. What is the resulting output waveform?




2 x 5 = 10

11) Describe the valence band, conduction band and forbidden energy gap with the help of energy level diagram.

12)

Find the output of the given circuit.

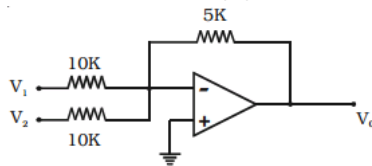

Section-E

4 x 10 = 40

13) Explain the working of a Colpitt's oscillator, with the neat circuit diagram.

14) Describe an operational amplifier. Explain its action as (i) Inverting amplifier (ii) Non-inverting amplifier.

15) a) Describe the CRO. Explain its parts.

(OR)

b) Explain the construction and working of a multimeter?
